$$\frac{35V}{160} = 2.1875A$$

$$\frac{35V}{16\Omega} = 2.1875A \qquad |_{\alpha}(0_{-}) = 2.19A_{\gamma}v_{\alpha}(0_{-}) = 0$$


$$V_{q}(0_{+}) = -10_{+} \cdot \frac{3s}{16} = -\frac{17s}{8} \qquad \gamma = \frac{L}{R} = \frac{13}{10}s$$


$$\gamma = \frac{L}{R} = \frac{13}{10} s$$

$$I_a(O_+) = \frac{35}{16} A$$

$$V_{\alpha}(+) = -\frac{175}{8} e^{-\frac{10+}{13}}$$
 $I_{\alpha}(+) = \frac{35}{16} e^{-\frac{10+}{13}}$
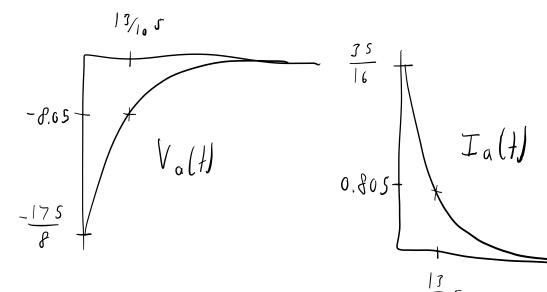
$$\mathcal{I}_{\alpha}(+) = \frac{35}{16} e^{-\frac{10+}{13}}$$



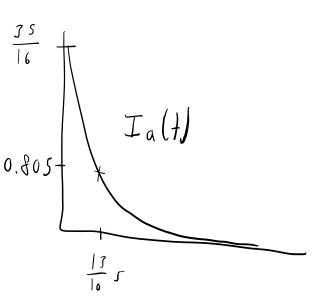

$$I_{\sigma}(\sigma_{\sigma}) =$$

$$\gamma = \frac{L}{R} = \frac{7}{4}$$

$$\frac{2}{I_{b}(0)} = 9A \quad V_{b}(0) = 0V \quad \gamma = \frac{L}{R} = \frac{7}{4}$$

$$I_{b}(1) = 9e^{-\frac{4+7}{7}} \quad V_{b}(0) = -9.8 = -72 \quad V_{b}(1) = -72e^{-\frac{4+7}{7}}$$

$$V_6(0_+) = -9.8 = -72$$

$$V_{b}(+) = -72e^{-\frac{4+}{7}}$$

