

Two Ways

September 22, 2024

1.

Superposition

When only the voltage source is connected and the current source is set to 0A, we can think of it as the current source is disconnected. This makes just 3 resistors in series which their equivalent resistance is $R_{eq} = R_1 + R_2 + R_3$.

Therefore the current through the resistors is $I = V_s / (R_1 + R_2 + R_3)$

Multiplying the current times the resistances, we get that

$$e_1 = (V_s \times (R_2 + R_3)) / (R_1 + R_2 + R_3), \text{ and that } e_2 = (V_s \times R_3) / (R_1 + R_2 + R_3)$$

Now calculating the circuit if $V_s = 0$ the equivalent resistance is $R_{eq} = R_1 || (R_2 + R_3)$ which expanded makes $1 / (1/R_1 + 1/(R_2 + R_3))$.

Therefore $e_1 = I_s / (1/R_1 + 1/(R_2 + R_3))$, simplifying to

$$e_1 = (I_s \times R_1 \times R_2 \times R_3) / ((R_2 \times R_3) + R_1)$$

Since $e_2 = (e_1 \times R_3) / (R_2 + R_3)$ we can substitute e_1 to get the equation $e_2 = (I_s \times R_1 \times R_2 \times R_3^2 \times (R_2 + R_3)) / ((R_2 \times R_3) + R_1)$.

Combining both of these, we get that

$$e_1 = (V_s \times (R_2 + R_3)) / (R_1 + R_2 + R_3) + (I_s \times R_1 \times R_2 \times R_3) / ((R_2 \times R_3) + R_1)$$

$$e_2 = (V_s \times R_3) / (R_1 + R_2 + R_3) + (I_s \times R_1 \times R_2 \times R_3^2 \times (R_2 + R_3)) / ((R_2 \times R_3) + R_1)$$

Nodal

With nodal analysis, we can come up with the two equations because we have two unknowns. $(V_s - e_1) / R_1 + I_s + (e_2 - e_1) / R_2 = 0$ and $e_2 / R_3 = (e_1 - e_2) / R_2$

Solving these two equations with some algebra gets us the solutions:

$$e_1 = (R_2 \times V_s + I_s \times R_1 \times R_2) / ((R_1 + R_2) - (R_1 \times R_2) / (R_2 + R_3))$$

$$e_2 = (R_2 \times R_3 \times (V_s + I_s \times R_1)) / ((R_2 + R_3) \times ((R_2 + R_1) - (R_1 \times R_3) / (R_2 + R_3)))$$

Equivalence

Rearranging the equations from the node and superposition analysis, they are the same.

2.

Superposition

Calculating when only I_1 is connected, we first find the equivalent resistance for the circuit, which is $R_{eq} = 75\Omega || 150\Omega = 50\Omega$

That means that $e_1 = I_1 \times 50$ and then we can treat each pair of resistors as voltage dividers to calculate e_2 and e_3

Therefore we get

$$e_2 = (I_1 \times 50 \times 45)/75 = I_1 \times 30 \text{ and } e_3 = (I_1 \times 50)/2 = I_1 \times 25$$

Calculating when only I_2 is connected, we can first calculate the current divider

$$\text{Current through the bottom will be } I_2 \times (105/225) = I_2 \times (7/15)$$

$$\text{Current through the top will be } I_2 \times (120/225) = I_2 \times (8/15)$$

$$\text{This means } e_3 = 75 \times I_2 \times (7/15) = I_2 \times 35 \text{ and}$$

$$e_2 = -45 \times I_2 \times (7/15) = -I_2 \times 21$$

Referencing e_1 from e_3 we can calculate

$$e_1 = I_2 \times 35 - 75 \times I_2 \times (8/15) \text{ and simplifying}$$

$$e_1 = -I_2 \times 5$$

Adding up the superpositions of I_1 and I_2 we get:

$$e_1 = 50I_1 - 5I_2$$

$$e_2 = 30I_1 - 21I_2$$

$$e_3 = 25I_1 + 35I_2$$

Nodal

Calculating with nodal analysis:

$$(e_1 - e_2)/30 = I_2 + e_2/45 \text{ and } (e_1 - e_3)/75 + I_2 = e_3/75 \text{ and}$$

$$I_1 = (e_1 - e_2)/30 + (e_1 - e_3)/75$$

After solving with algebra:

$$e_1 = 50I_1 - 5I_2$$

$$e_2 = 30I_1 - 21I_2$$

$$e_3 = 25I_1 + 35I_2$$

Equivalence

These are the same